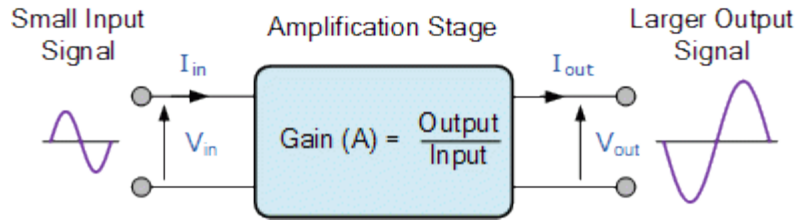


Introduction to the Amplifier

An amplifier is an electronic device or circuit which is used to increase the magnitude of the signal applied to its input



Amplifier is the generic term used to describe a circuit which produces an increased version of its input signal. Amplifier circuits are different and they are classified according to their circuit configurations and modes of operation.

Generally, amplifiers can be sub-divided into two distinct types depending upon their power or voltage gain. One type is called the **Small Signal Amplifier** which include pre-amplifiers, instrumentation amplifiers etc. Small signal amplifiers are designed to amplify very small signal voltage levels of only a few micro-volts (μV) from sensors or audio signals.

The other type are called **Large Signal Amplifiers** such as audio power amplifiers or power switching amplifiers. Large signal amplifiers are designed to amplify large input voltage signals or switch heavy load currents as you would find driving loudspeakers.

In general the classification of an amplifier depends upon the size of the signal, large or small, its physical configuration and how it processes the input signal

The type or classification of an Amplifier is given in the following table.

Classification of Signal Amplifier

Type of Signal	Type of configuration	Classification	Frequency of operation
Small	Common Emitter	Class A	DC Current
Large	Common Base	Class B	Audio frequency(AF)
	Common collector	Class AB	Radio frequency(RF)
	---do----	Class C	HF,UHF &SHF

Important Points to remember:

An ideal signal amplifier will have three main properties: Input Resistance or (R_{IN}), Output Resistance or (R_{OUT}) and of course amplification known commonly as Gain or (A).

Voltage Amplifier Gain

$$\text{Voltage Gain } (A_v) = \frac{\text{Output Voltage}}{\text{Input Voltage}} = \frac{V_{out}}{V_{in}}$$

Current Amplifier Gain

$$\text{Current Gain } (A_i) = \frac{\text{Output Current}}{\text{Input Current}} = \frac{I_{out}}{I_{in}}$$

Power Amplifier Gain

$$\text{Power Gain } (A_p) = A_v \times A_i$$

Note that for the Power Gain you can also divide the power obtained at the output with the power obtained at the input. Also when calculating the gain of an amplifier, the subscripts v, i and p are used to denote the type of signal gain being used.

The power gain (A_p) or power level of the amplifier can also be expressed in **Decibels, (dB)**. The Bel (B) is a logarithmic unit (base 10) of measurement that has no units. Since the Bel is too large a unit of measure, it is prefixed with *deci* making it **Decibels** instead with one decibel being one tenth (1/10th) of a Bel. To calculate the gain of the amplifier in Decibels or dB, we can use the following expressions.

- Voltage Gain in dB: $a_v = 20 \cdot \log(A_v)$
- Current Gain in dB: $a_i = 20 \cdot \log(A_i)$
- Power Gain in dB: $a_p = 10 \cdot \log(A_p)$

Note that the DC power gain of an amplifier is equal to ten times the common log of the output to input ratio, where as voltage and current gains are 20 times the common log of the ratio. Note however, that 20dB is not twice as much power as 10dB because of the log scale.

Amplifier Example

Determine the Voltage, Current and Power Gain of an amplifier that has an input signal of 1mA at 10mV and a corresponding output signal of 10mA at 1V. Also, express all three gains in decibels, (dB).

The Various Amplifier Gains:

$$A_v = \frac{\text{Output Voltage}}{\text{Input Voltage}} = \frac{1}{0.01} = 100$$

$$A_i = \frac{\text{Output Current}}{\text{Input Current}} = \frac{10}{1} = 10$$

$$A_p = A_v \times A_i = 100 \times 10 = 1,000$$

Amplifier Gains given in Decibels (dB):

$$a_v = 20 \log A_v = 20 \log 100 = 40 \text{ dB}$$

$$a_i = 20 \log A_i = 20 \log 10 = 20 \text{ dB}$$

$$a_p = 10 \log A_p = 10 \log 1000 = 30 \text{ dB}$$

Then the amplifier has a Voltage Gain, (A_v) of 100, a Current Gain, (A_i) of 10 and a Power Gain, (A_p) of 1,000

Ideal Amplifier

We can now specify the characteristics for an ideal amplifier from our discussion above with regards to its **Gain**, meaning voltage gain:

- The amplifier's gain, (A) should remain constant for varying values of input signal.
- Gain is not affected by frequency. Signals of all frequencies must be amplified by exactly the same amount.
- The amplifier's gain must not add noise to the output signal. It should remove any noise that is already present in the input signal.
- The amplifier's gain should not be affected by changes in temperature giving good temperature stability.
- The gain of the amplifier must remain stable over long periods of time.

Definition and distinction or details of class of amplifiers.

- Amplifier classification takes into account the portion of the input signal in which the output transistor conducts as well as determining both the efficiency and the amount of power that the switching transistor both consumes and dissipates in the form of wasted heat.


The most commonly used being:

- Class A Amplifier – has low efficiency of less than 40% but good signal reproduction and linearity.
- Class B Amplifier – is twice as efficient as class A amplifiers with a maximum theoretical efficiency of about 70% because the amplifying device only conducts (and uses power) for half of the input signal.
- Class AB Amplifier – has an efficiency rating between that of Class A and Class B but poorer signal reproduction than Class A amplifiers.
- Class C Amplifier – is the most efficient amplifier class but distortion is very high as only a small portion of the input signal is amplified therefore the output signal bears very little resemblance to the input signal. Class C amplifiers have the worst signal reproduction.

Class A Amplifier Operation

Class A Amplifier operation is where the entire input signal waveform is faithfully reproduced as the transistor is perfectly biased within its active region. This means that the switching transistor is never driven into its cut-off or saturation regions. The result is that the AC input signal is perfectly “centred” between the amplifier's upper and lower signal limits as shown below.

Class A Amplifier Output Waveform

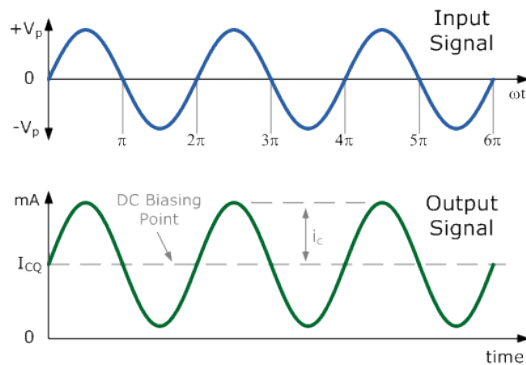

A Class-A amplifier configuration uses the same switching transistor for both halves of the output waveform and due to its central biasing arrangement, the output transistor always has a constant DC biasing current, (I_{CQ}) flowing through it, even if there is no input signal present. In other words the output transistors never turns "OFF" and is in a permanent state of idle. hence it requires a heat sink as DC is lost as heat.


Class B Amplifier Operation

The **Class-B Amplifier** uses two complimentary transistors (either an NPN and a PNP or a NMOS and a PMOS) to amplify each half of the output waveform.

One transistor conducts for only one-half of the signal waveform while the other conducts for the other or opposite half of the signal waveform. This means that each transistor spends half of its time in the active region and half its time in the cut-off region thereby amplifying only 50% of the input signal.

Therefore with zero input signal there is zero output. As only half the input signal is presented at the amplifiers output this improves the amplifier efficiency over the previous Class-A configuration as shown below.

Class B Amplifier Output Waveform

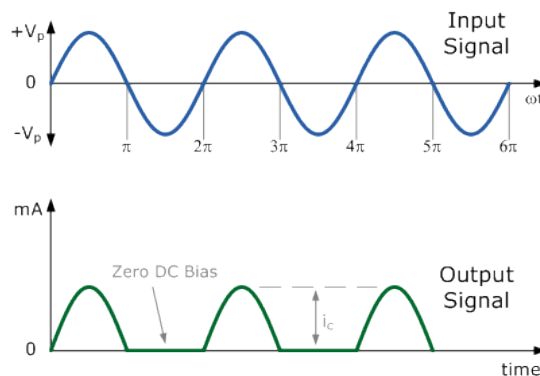


Class AB Amplifier Operation

The **Class-AB Amplifier** is a compromise between the Class-A and the Class-B configurations above. While Class-AB operation still uses two complementary transistors in its output stage a very small biasing voltage is applied to the Base of each transistor to bias them close to their cut-off region when no input signal is present.

An input signal will cause the transistor to operate as normal within its active region, eliminating any crossover distortion which is always present in the class-B configuration. A small biasing Collector current (I_{CQ}) will flow through the transistor when there is no input signal present, but generally it is much less than that for the Class-A amplifier configuration.

Thus each transistor is conducting, "ON" for a little more than half a cycle of the input waveform. The small biasing of the Class-AB amplifier configuration improves both the efficiency and linearity of the amplifier circuit compared to a pure Class-A configuration above.

Class AB Amplifier Output Waveform

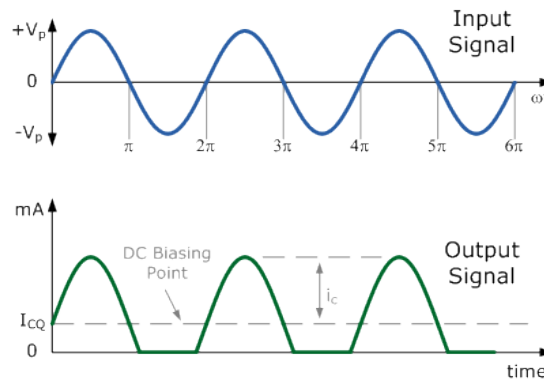

Here we can make a comparison between the most common types of amplifier classifications in the following table.

Power Amplifier Classes

Class	A	B	C	AB
Conduction Angle	360°	180°	Less than 90°	180 to 360°
Position of the Q-point	Centre Point of the Load Line	Exactly on the X-axis	Below the X-axis	In between the X-axis and the Centre Load Line

Overall Efficiency	Poor 25 to 30%	Better 70 to 80%	Higher than 80%	Better than A but less than B 50 to 70%
Signal Distortion	None if Correctly Biased	At the X-axis Crossover Point	Large Amounts	Small Amounts

OPTIONAL(Badly designed amplifiers especially the Class "A" types may also require larger power transistors, more expensive heat sinks, cooling fans, or even an increase in the size of the power supply required to deliver the extra wasted power required by the amplifier. Power converted into heat from transistors, resistors or any other component for that matter, makes any electronic circuit inefficient and will result in the premature failure of the device.

So why use a Class A amplifier if its efficiency is less than 40% compared to a Class B amplifier that has a higher efficiency rating of over 70%. Basically, a Class A amplifier gives a much more linear output meaning that it has, **Linearity** over a larger frequency response even if it does consume large amounts of DC power.)

In this **Introduction to the Amplifier** tutorial, we have seen that there are different types of amplifier circuit each with its own advantages and disadvantages. In the next tutorial about amplifiers, we will look at the most commonly connected type of transistor amplifier circuit, the common emitter amplifier. Most transistor amplifiers are of the Common Emitter or CE type circuit due to their large gains in voltage, current and power as well as their excellent input/output characteristics.