

## Transistor as a Amplifier

Transistors are can be configured in three different ways depending on whether the common terminal b/w the input and output ports is base, collector or emitter and are named common base(CB), common collector(CC) and common emitter(CE), accordingly.


These can be used as switches or amplifiers based on the choice of OPERATING POINT AND REGION OF OPERATION .For switching the transistor circuits when made to operate between cut-off and saturation regions and for amplifiers when made to operate in their active region.

In addition, it is to be kept in mind that the transistors are inherently nothing but the current-controlled devices wherein a small change in the base current,  $I_B$  results in a large variation in the collector current,  $I_C$  s.t.

( $I_E = I_B + I_C$ ).

Figure 1 shows a simple common emitter circuit which uses an npn transistor whose

- Collector terminal (output terminal) is connected to supply voltage  $V_{CC}$  through the collector resistor  $R_C$ .
- Base terminal is provided with the AC signal which needs to be amplified.
- Emitter terminal is grounded (hence also referred to as Grounded Emitter configuration).

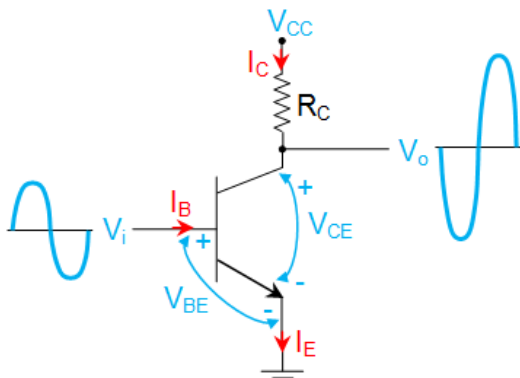

**Figure 1 A Simple Common Emitter Amplifier**

1). For 1<sup>st</sup> half of input signal, as the input voltage  $V_i$  increases, the base current  $I_B$  also increases which in turn increases the collector current  $I_C$ .

This causes an increase in the voltage drop across the collector resistor,  $R_C$  which results in a decreased output voltage  $V_0$  as emphasized by the following relationship


$$V_0 = V_{CC} - I_C R_C$$

2). For the 2<sup>nd</sup> half of the input signal the input voltage goes on decreasing,  $I_B$  and hence  $I_C$  decrease, due to which the voltage drop across  $R_C$  also decreases thereby increasing the output voltage.

3). Thus for the positive half-cycle of the input waveform, one would get amplified negative half-cycle while for the negative input signal, the output would be a amplified positive pulse. Hence there exists a phase-shift of  $180^\circ$  between the input and the output waveforms of the **common emitter amplifier (also called as inverting amplifier)**.

### Faithful, Undistorted or practical amplifier

However in order to obtain an faithful(undistorted) amplification gain the transistor needs to be biased properly by setting a suitable operating point (Q-point). This indicates that practically one has to resort to a stable network (Figure 2) which will be resistant to the changes in temperature and other transistor parameters.

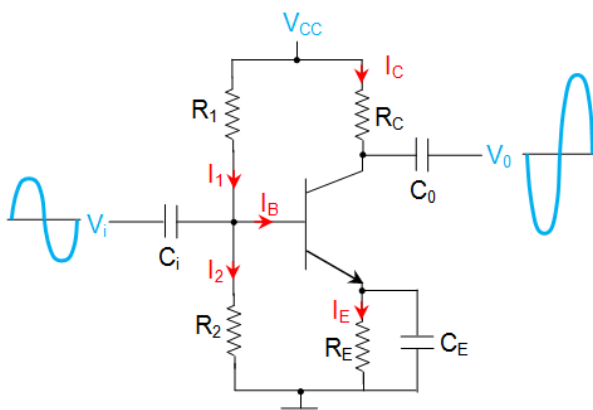

**Figure 2 Common Emitter Amplifier with Biasing and Decoupling Details**

## CONSTRUCTION

- 1).The resistors  $R_1$  and  $R_2$  are used to provide bias for the base of the transistor (voltage-divider transistor biasing)
- 2).The emitter resistor  $R_E$  is used to ensure that proper DC conditions are maintained for the circuit by regulating the amount of DC feedback.
- 3). The capacitors  $C_i$  and  $C_o$  which are the decoupling capacitors used to provide AC coupling between the amplifier stages or blocks the DC from entering or leaving the ckt. The values of these capacitances are chosen to such that they provide negligible reactance at the frequency of operation.

**OPTIONAL FOR STUDENTS** may skip this technical settings(In particular, the value of the input capacitance  $C_i$  should be chosen to be equal to the resistance of the input circuit at the lowest frequency such that it results in a -3dB fall at this frequency. In addition, the value of the output capacitor  $C_o$  is chosen so that it is equal to the circuit resistance at the lowest operating frequency.)

Further the emitter voltage  $V_E$  is chosen to be 10% of the supply voltage  $V_{CC}$  to ensure a good level of DC stability and the current through  $R_1$  which is  $I_1$  is chosen to be 10 times the required base current. Here it is to be noted that, even  $I_2$  will be of almost the same value as the base current  $I_b$  will be negligible.

- 4).The emitter bypass capacitor  $C_E$  when added into the circuit, increases its gain considerably by short-circuiting the emitter resistance  $R_E$  for high frequency signals, which results in the reduction of the overall transistor load. **OPTIONAL**(The value of this  $C_E$  is chosen such that the capacitor offers a reactance value which is equal to the  $1/10^{\text{th}}$  of  $R_E$  at the lowest operating frequency.)

**Mathematical expression**  $\beta$ =gain factor for CE mode and  $A_V$  is Voltage gain.

$$\beta = \frac{I_C}{I_B}$$

*and*

$$A_V = \frac{V_0}{V_i} = -\frac{R_C}{R_E}$$

These **common emitter amplifiers** are most widely used, say for example as low noise amplifiers and radio frequency amplifiers, as they offer medium input resistance, medium output resistance, medium voltage gain, medium current gain and high power gain.

IMP: The analysis of the ckt by means of h(hybrid parameters is to be done from book). The discussion is quite explanatory. I will not upload any other method/mathematical formulation to avoid confusion .will send pic of the same with written explanations wherever necessary.